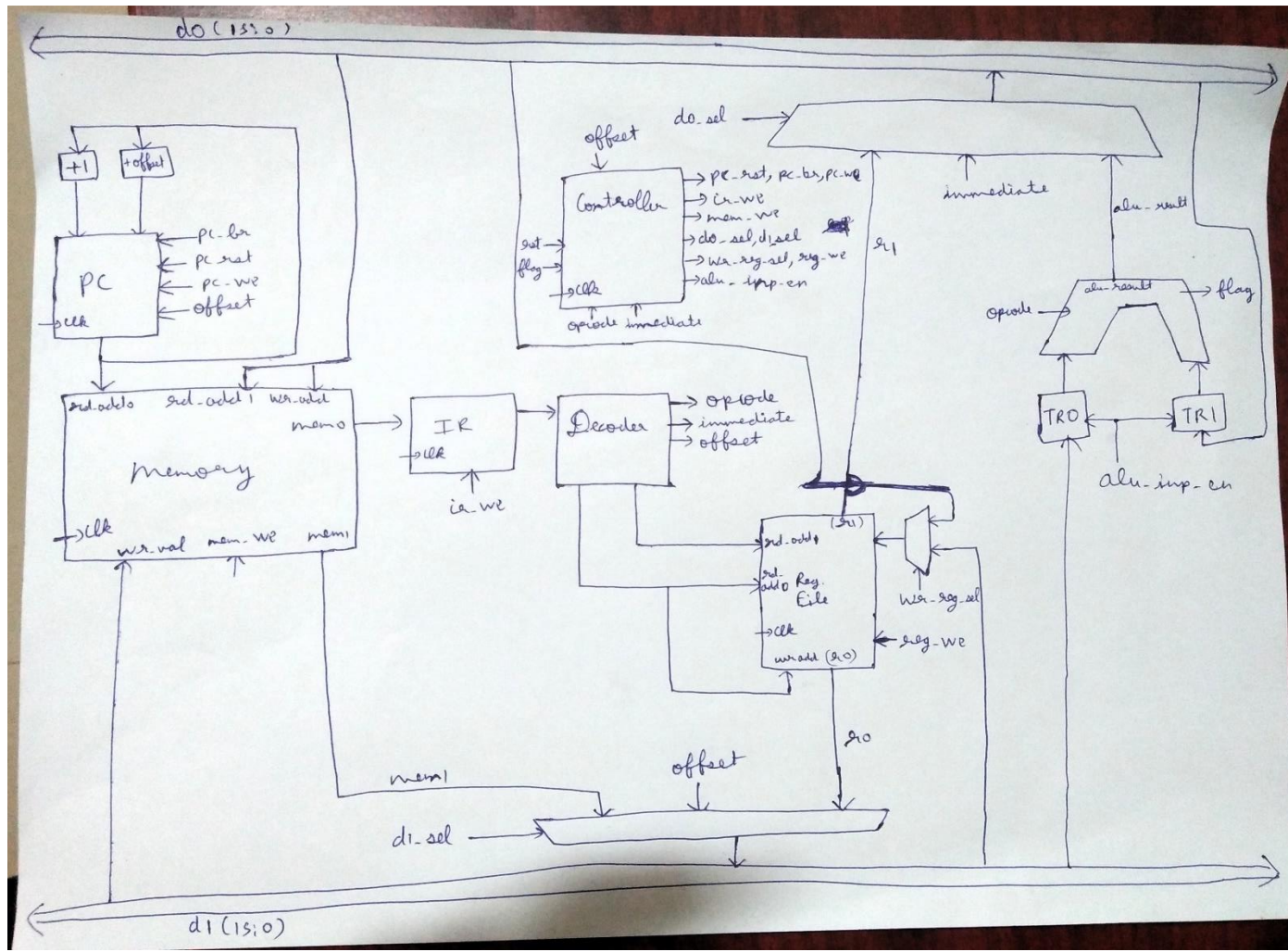


Name: Gaurav Somani


Sr. No. 16082

Course : M.Tech (CeNSE)

Block schematic of the datapath



FSM of Controller

 

FSM of the controller is expressed in the VHDL process below with the states shown in above diagram

```
fsm: process (ar,br,im,op,flag,pr_state,clk)
```

```
begin
```

```
case pr_state is
```

```
when s_rst =>
```

```
    pc_br <= '-'; pc_rst <='1'; pc_we <= '0';
```

```
    mem_we <= '0';ir_we <= '0';reg_we <= '0';
```

```
    d0_sel <= "--"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '-';
```

```
    nx_state <=s_fetch;
```

```
when s_fetch =>
```

```
    pc_rst <='0'; pc_we <= '0';
```

```
    mem_we <= '0';ir_we <= '1';reg_we <= '0';
```

```
    d0_sel <= "--"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0'; wr_reg_sel <= '-';
```

```
    nx_state <=s_decode;
```

```
when s_decode =>
```

```
    pc_br <= '-'; pc_rst <='0'; pc_we <= '0';
```

```
    mem_we <= '0';ir_we <= '0';reg_we <= '0';
```

```
    d0_sel <= "--"; d1_sel <= "--"; alu_inp_en <= '0'; wr_reg_sel <= '0';done <= '0';
```

```
    if(ar = '1' or br = '1') then
```

```
        nx_state <= s_alu_bin ;
```

```
    elsif( im = '1' ) then
```

```
        nx_state <= s_alu_im;
```

```
    elsif( op = load or op = store ) then
```

```
        nx_state <= s_alu_ofs;
```

```
    elsif( op = lui ) then
```

```
        nx_state <= s_lui;
```

```
    elsif( op = mov ) then
```

```
        nx_state <= s_mov;
```

```
    else
```

```
        nx_state <= s_done;
```

```
    end if;
```

when s_mov =>

```
pc_br <= '0'; pc_rst <='0'; pc_we <= '1';  
mem_we <= '0';ir_we <= '0';reg_we <= '1';  
d0_sel <= "01"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '0';  
nx_state <= s_fetch;
```

when s_alu_bin =>

```
pc_rst <='0';pc_br <= '0'; pc_we <='0';  
mem_we <= '0';ir_we <= '0';reg_we <= '0';  
d0_sel <= "01"; d1_sel <= "00"; done <= '0';alu_inp_en <= '1';wr_reg_sel <= '0';  
if(br='1') then  
    nx_state <= s_branch;  
else  
    nx_state <= s_store_alu;  
end if;
```

when s_branch =>

```
pc_rst <='0'; pc_we <= '1';  
mem_we <= '0';ir_we <= '0';reg_we <= '0';  
d0_sel <= "--"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '0';  
if(flag = '1') then  
    pc_br <= '1';  
else  
    pc_br <= '0';  
end if;  
nx_state <= s_fetch;
```

when s_lui =>

```
pc_br <= '0'; pc_rst <='0'; pc_we <= '1';  
mem_we <= '0';ir_we <= '0';reg_we <= '1';  
d0_sel <= "10"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '0';  
nx_state <= s_fetch;
```

when s_alu_im =>

```
pc_br <= '-'; pc_rst <='0'; pc_we <= '0';  
mem_we <= '0';ir_we <= '0';reg_we <= '0';  
d0_sel <= "10"; d1_sel <= "00"; done <= '0';alu_inp_en <= '1';wr_reg_sel <= '-';  
nx_state <= s_store_alu;
```

when s_alu_ofs =>

```
pc_br <= '-'; pc_rst <='0'; pc_we <= '0';  
mem_we <= '0';ir_we <= '0';reg_we <= '0';  
d0_sel <= "01"; d1_sel <= "01"; done <= '0';alu_inp_en <= '1';wr_reg_sel <= '-';  
if(op = load) then  
    nx_state <= s_load;  
else  
    nx_state <= s_store_mem;  
end if;
```

when s_store_alu =>

```
pc_br <= '0'; pc_rst <='0'; pc_we <= '1';  
mem_we <= '0';ir_we <= '0';reg_we <= '1';  
d0_sel <= "00"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '0';  
nx_state <= s_fetch;
```

when s_load =>

```
pc_br <= '-'; pc_rst <='0'; pc_we <= '0';  
mem_we <= '0';ir_we <= '0';reg_we <= '0';  
d0_sel <= "00"; d1_sel <= "--"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '-';  
nx_state <= s_load_mem;
```

when s_load_mem =>

```
pc_br <= '0'; pc_rst <='0'; pc_we <= '1';  
mem_we <= '0';ir_we <= '0';reg_we <= '1';  
d0_sel <= "--"; d1_sel <= "10"; done <= '0';alu_inp_en <= '0';wr_reg_sel <= '1';  
nx_state <= s_fetch;
```

```
when s_store_mem =>
```

```
    pc_br <= '0'; pc_rst <='0'; pc_we <= '1';
```

```
    mem_we <= '1'; ir_we <= '0'; reg_we <= '0';
```

```
    d0_sel <= "00"; d1_sel <= "00"; done <= '0'; alu_inp_en <= '0'; wr_reg_sel <= '-';
```

```
    nx_state <= s_fetch;
```

```
when s_done =>
```

```
    pc_br <= '-'; pc_rst <='0'; pc_we <= '0';
```

```
    mem_we <= '0'; ir_we <= '0'; reg_we <= '0';
```

```
    d0_sel <= "--"; d1_sel <= "--"; done <= '1'; alu_inp_en <= '0'; wr_reg_sel <= '-';
```

```
    nx_state <= s_done;
```

```
when others =>
```

```
    pc_br <= '-'; pc_rst <='-'; pc_we <= '-';
```

```
    mem_we <= '0'; ir_we <= '0'; reg_we <= '0';
```

```
    d0_sel <= "--"; d1_sel <= "--"; done <= '0'; alu_inp_en <= '0'; wr_reg_sel <= '-';
```

```
    nx_state <= s_rst;
```

```
end case;
```

```
end process fsm;
```

Timing Report

Clock Frequency : 100 MHz

Duty Cycle = 50 %

Setup	Hold	Pulse Width
Worst Negative Slack (WNS): 3.518 ns	Worst Hold Slack (WHS): 0.107 ns	Worst Pulse Width Slack (WPWS): 4.500 ns
Total Negative Slack (TNS): 0.000 ns	Total Hold Slack (THS): 0.000 ns	Total Pulse Width Negative Slack (TPWS): 0.000 ns
Number of Failing Endpoints: 0	Number of Failing Endpoints: 0	Number of Failing Endpoints: 0
Total Number of Endpoints: 1427	Total Number of Endpoints: 1427	Total Number of Endpoints: 746

All user specified timing constraints are met.

Utilisation

Name	Slice LUTs (20800)	Slice Registers (41600)	F7 Muxes (16300)	Bonded IOB (106)	BUFGCTRL (32)
io_ctl	617	762	192	19	1
cp (cpu)	617	762	192	0	0
al (alu)	6	0	0	0	0
ctl (con)	276	5	80	0	0
pr_cou	144	5	64	0	0
reg_file	191	160	48	0	0